



POWERFACTORY

PowerFactory 2021

Technical Reference

Series RLC-Filter
ElmSfilt

PF2021

POWER SYSTEM SOLUTIONS
MADE IN GERMANY

Publisher:

DlgSILENT GmbH
Heinrich-Hertz-Straße 9
72810 Gomaringen / Germany
Tel.: +49 (0) 7072-9168-0
Fax: +49 (0) 7072-9168-88
info@digsilent.de

Please visit our homepage at:
<https://www.digsilent.de>

Copyright © 2020 DlgSILENT GmbH

All rights reserved. No part of this
publication may be reproduced or
distributed in any form without written
permission of DlgSILENT GmbH.

December 1, 2020
PowerFactory 2021
Revision 1

Contents

1 General Description	1
2 Load Flow Analysis	1
2.1 Balanced AC Load Flow	1
2.1.1 Zero Capacitance	3
2.1.2 Input Parameters	3
2.1.3 Calculation Parameters	3
2.2 Unbalanced AC Load Flow	4
3 Short Circuit	4
4 RMS-Simulation	5
5 EMT-Simulation	5
5.1 Signals	6
6 Harmonics/Power Quality	6
6.1 Balanced Calculation	6
6.2 Unbalanced Calculation	7
List of Figures	8
List of Tables	9

1 General Description

The series RLC-filter model is implemented as a single-tuned filter (series RLC circuit), as shown in Figure 1.1.



Figure 1.1: Series RLC-Filter element

The general parameters of the series RLC-filter are defined in Table 1.1

Table 1.1: General input parameters

Parameter	Default Value	Description	Range
loc_name		Name	
bus1		Terminal (StaCubic)	
bus1_bar		Terminal	
cpZone		Zone	
cpArea		Area	
outserv	0	Out of Service	$0 \leq x \leq 1$
ratings			
pRating		Thermal Rating	
systyp	AC	System Type	AC
nphases	3	No. of Phases	1:3

2 Load Flow Analysis

There are two different models:

- Model for balanced calculations
- Model for unbalanced calculations

2.1 Balanced AC Load Flow

In Balanced Load Flow, the following model is used:

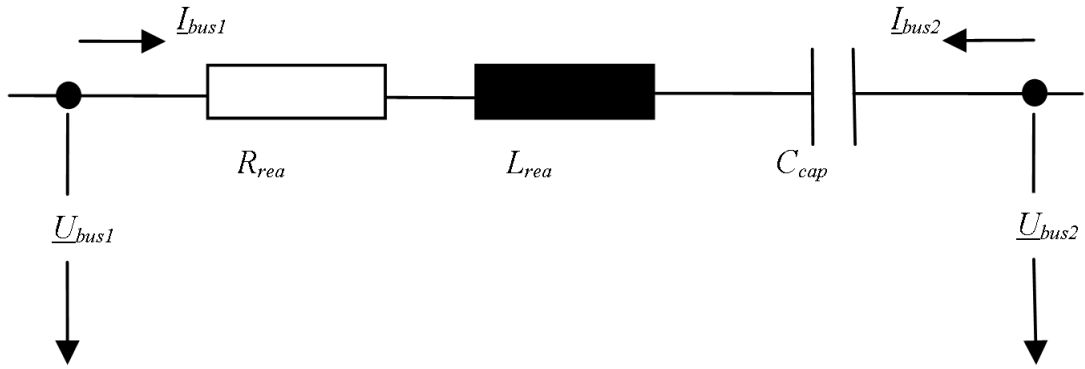


Figure 2.1: Balanced Load Flow Model

Where:

- R_{rea} is the resistance in Ω
- L_{rea} is the reactance in mH
- C_{cap} is the susceptance in μF

From these values, we can obtain the reactance and susceptance values:

- $X_{rea} = 2\pi f \cdot L_{rea} \cdot 1e^{-3}$ is the reactance in Ω
- $B_{cap} = 2\pi f \cdot C_{cap} \cdot 1e^{-6}$ is the susceptance in S
- f is the network frequency in Hz

The initialisation of the impedance is calculated as follows:

$$\underline{Z}_{rl} = R_{rea} + jX_{rea} \quad (1)$$

$$X_{cap} = \frac{1}{B_{cap}} \quad (2)$$

$$\underline{Z} = \underline{Z}_{rl} - jX_{cap} \quad (3)$$

The equations for voltage and current are:

$$\underline{U}_{bus1} - \underline{U}_{bus2} = \underline{I}_1 \cdot \underline{Z} \quad (4)$$

$$\underline{I}_{bus1} + \underline{I}_{bus2} = 0 \quad (5)$$

Where:

- \underline{U}_{bus1} is the line to ground voltage in terminal 1 in kV
- \underline{U}_{bus2} is the line to ground voltage in terminal 2 in kV

- \underline{I}_{bus1} is the current in terminal 1 in kA
- \underline{I}_{bus2} is the current in terminal 2 in kA

The voltage across the capacitor, u_c in p.u. is calculated as follows:

$$u_c = \left| \frac{\underline{U}_{bus1} - \underline{U}_{bus2} - \underline{I}_{bus1} \cdot \underline{Z}_{rl}}{\underline{U}_{bus1}} \right|$$

2.1.1 Zero Capacitance

If the value for C_{cap} is zero, the series filter is modelled as a R-L circuit, and in such a case, the initialization of the impedance is calculated as follows:

$$\begin{aligned}\underline{Z}_{rl} &= R_{rea} + j X_{rea} \\ \underline{Z} &= \underline{Z}_{rl}\end{aligned}$$

The equations for voltage and current are the same as 4 and 5.

2.1.2 Input Parameters

The input parameters for balanced Load Flow calculation are defined in Table 2.1.

Table 2.1: Input parameters for balanced load flow

Parameter	Unit	Default Value	Description	Symbol
rrea	mH		Resistance	R_{rea}
lrea	Ω		Inductance	L_{rea}
ccap	μF		Capacitance	C_{cap}

2.1.3 Calculation Parameters

The calculation parameters used in the RMS model are presented in Table 2.2.

Table 2.2: Calculation parameters for balanced load flow

Parameter	Unit	Description	Symbol
Zrl	Ω	Shunt Impedance	\underline{Z}_{rl}
Xcap	Ω	Capacitor Reactance	X_{cap}
frnom	Hz	Nominal Frequency	f
hpi	rad/s	Nominal Angular Frequency	$2\pi f$
uc	p.u.	Voltage across Capacitor	u_c

2.2 Unbalanced AC Load Flow

In Balanced Load Flow, the following model is used:

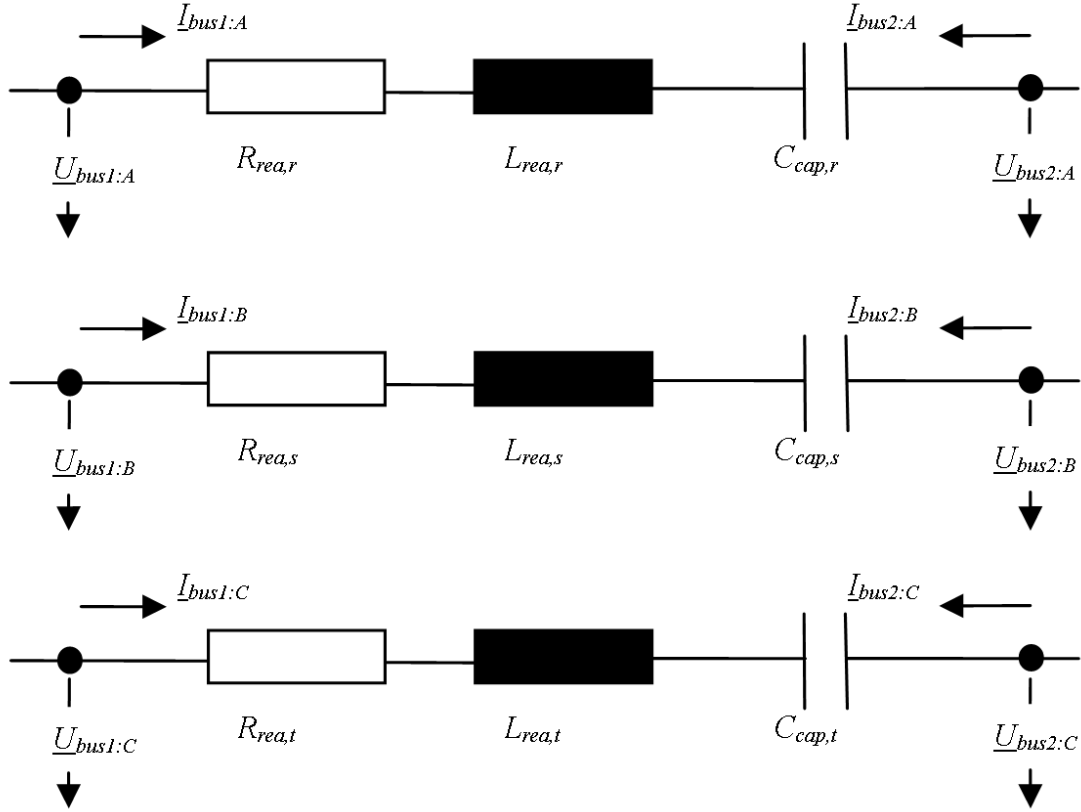


Figure 2.2: Unbalanced Load Flow Model

The parameters are as follows:

$$\begin{aligned} R_{rea:r} &= R_{rea:s} = R_{rea:t} = R_{rea} \\ L_{rea:r} &= L_{rea:s} = L_{rea:t} = L_{rea} \\ C_{cap:r} &= C_{cap:s} = C_{cap:t} = C_{rea} \end{aligned}$$

The equations for impedance, voltage and current for each phase are the same as those described in 1 to 5.

3 Short Circuit

The equations for short-circuit are the same used for load flow explained in Section 2.

4 RMS-Simulation

The equations for short-circuit are the same used for load flow explained in Section 2.

5 EMT-Simulation

In EMT Simulation, the following model is used:

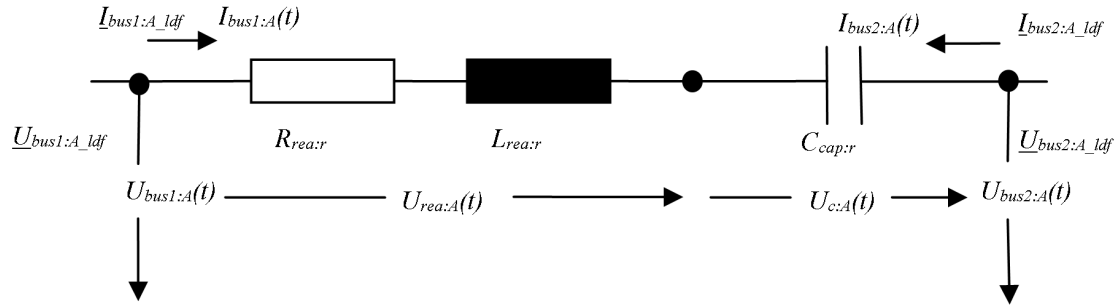


Figure 5.1: EMT Model

The parameters are as follows:

$$\begin{aligned} R_{rea:r} &= R_{rea:s} = R_{rea:t} = R_{rea} \\ L_{rea:r} &= L_{rea:s} = L_{rea:t} = L_{rea} \\ C_{cap:r} &= C_{cap:s} = C_{cap:t} = C_{rea} \end{aligned}$$

The initialisation of the equations for voltage and current are presented below:

$$\begin{aligned} U_{c:A}(0) &= \Re\{U_{bus1:A_ldf} - U_{bus2:A_ldf} - I_{bus1:A_ldf} \cdot (R_{rea:r} + j2\pi f \cdot L_{rea:r})\} \\ U_{c:B}(0) &= \Re\{U_{bus1:B_ldf} - U_{bus2:B_ldf} - I_{bus1:B_ldf} \cdot (R_{rea:s} + j2\pi f \cdot L_{rea:s})\} \\ U_{c:C}(0) &= \Re\{U_{bus1:C_ldf} - U_{bus2:C_ldf} - I_{bus1:C_ldf} \cdot (R_{rea:t} + j2\pi f \cdot L_{rea:t})\} \\ \frac{d(U_{c:A}(0))}{dt} &= \Re\{j2\pi f \cdot U_{c:A}(0)\} \\ \frac{d(U_{c:B}(0))}{dt} &= \Re\{j2\pi f \cdot U_{c:B}(0)\} \\ \frac{d(U_{c:C}(0))}{dt} &= \Re\{j2\pi f \cdot U_{c:C}(0)\} \end{aligned}$$

Finally, the equations for voltage and current in the series RLC-filter are:

$$\begin{aligned}
U_{c:r}(t) &= U_{bus1:A}(t) - U_{bus2:A}(t) - R_{rea:r} \cdot I_{bus1:A}(t) - L_{rea:r} \cdot \frac{d(I_{bus1:A}(t))}{dt} \\
U_{c:s}(t) &= U_{bus1:B}(t) - U_{bus2:B}(t) - R_{rea:s} \cdot I_{bus1:B}(t) - L_{rea:s} \cdot \frac{d(I_{bus1:B}(t))}{dt} \\
U_{c:t}(t) &= U_{bus1:C}(t) - U_{bus2:C}(t) - R_{rea:t} \cdot I_{bus1:C}(t) - L_{rea:t} \cdot \frac{d(I_{bus1:C}(t))}{dt} \\
I_{bus1:A}(t) &= C_{cap:r} \cdot \frac{d(U_{c:r}(t))}{dt} \\
I_{bus1:B}(t) &= C_{cap:s} \cdot \frac{d(U_{c:s}(t))}{dt} \\
I_{bus1:C}(t) &= C_{cap:t} \cdot \frac{d(U_{c:t}(t))}{dt} \\
I_{bus1:A}(t) + I_{bus2:A}(t) &= 0 \\
I_{bus1:B}(t) + I_{bus2:B}(t) &= 0 \\
I_{bus1:C}(t) + I_{bus2:C}(t) &= 0
\end{aligned}$$

5.1 Signals

The signals available in EMT simulation are presented in Table 5.1.

Table 5.1: *ElmSfilt* Signals (EMT-Simulation)

Parameter	Unit	IN/OUT	Description	Symbol
U_ca	kV	STATE	Voltage Across Capacitor, Phase A	$U_{c:A}$
U_cb	kV	STATE	Voltage Across Capacitor, Phase B	$U_{c:B}$
U_cc	kV	STATE	Voltage Across Capacitor, Phase C	$U_{c:C}$

6 Harmonics/Power Quality

The equations for voltage and current are the same as those described in Section 2, with the parameters calculated as described in the sections below.

In addition, frequency-dependent characteristics may be defined for the following parameters (parameter names follow in parentheses): R (*rrea*), L (*lrea*) and C (*ccap*).

Note: For absolute characteristics, the values defined in the element (not in the characteristic) will be used at the fundamental frequency.

6.1 Balanced Calculation

The parameters are as follows:

$$\underline{Z}_{rl} = R_{rea} + jX_{rea} \cdot f_{harm} \quad (6)$$

$$X_{cap} = \frac{1}{B_{cap}} \cdot f_{harm} \quad (7)$$

$$\underline{Z} = \underline{Z}_{rl} - jX_{cap} \quad (8)$$

Where f_{harm} is the harmonic order.

6.2 Unbalanced Calculation

The equations for impedance for each phase are the same as those described in 6 to 8.

List of Figures

1.1	Series RLC-Filter element	1
2.1	Balanced Load Flow Model	2
2.2	Unbalanced Load Flow Model	4
5.1	EMT Model	5

List of Tables

1.1	General input parameters	1
2.1	Input parameters for balanced load flow	3
2.2	Calculation parameters for balanced load flow	3
5.1	<i>ElmSfilt</i> Signals (EMT-Simulation)	6